



UNIVERSITY OF TEHRAN

Report for Computer Assignment 3


RT Level Components, Iterative Logic, Synthesis

Instructor : Dr. Navabi

Danial Saeedi

Problem 1

Circuit Diagram

 

Calculating Delay Values

AND Gate Delay

In computer Assignment 1, we calculated the worst-case delay of NAND gate. (To 1 = 10ns, To 0 = 8ns, Avg = 9ns)

Delay values for NOT gate are #(5,6). (Avg = 5ns)

If we invert a NAND gate, we get AND gate. So the AND gate delay is $5 + 9 = 14\text{ns}$.


OR Gate Delay

Delay values for NOR gate is #(10,14). (Avg = 12ns)

If we invert a NOR gate, we get OR gate. So the OR gate delay is $12 + 5 = 17\text{ns}$

XOR Gate Delay

 The XOR gate delay is $9 + 9 + 5 = 23\text{ns}$



Worst-case delay of FA

The sum output comes from two consecutive XOR gates. So worst-case delay for S is $23 + 23 = 46$

The longest path from input to carry-out(co) includes AND, OR gate. So worst-case delay for CO is $14 + 17 = 31$

So the worst-case delay for FA is 46ns.

Verilog Code


Structural implementation of FA :

```
1 `timescale 1ns/1ns
2 module FA_structural(input a,b,cin,output s,co);
3     wire w1,w2,w3;
4     xor #23 g1(w1,a,b);
5     xor #23 g2(s,w1,cin);
6     and #14 g3(w2,w1,cin);
7     and #14 g4(w3,a,b);
8     or #17 g5(co,w2,w3);
9 endmodule
```

Testbench

```
1 `timescale 1ns/1ns
2 module FA_structural_TB();
3     reg aa,bb,ccin;
4     wire cout,sum;
5     FA_structural CUT1(aa,bb,ccin,sum,cout);
6
7     initial begin
8         #10 aa = 1; bb = 1; ccin = 1;
9         #80 aa = 1; bb = 0; ccin = 0;
10        #80 aa = 1; bb = 1; ccin = 0;
11        #80 aa = 1; bb = 0; ccin = 0;
12        #80 aa = 1; bb = 0; ccin = 1;
13        #80 aa = 0; bb = 0; ccin = 0;
14        #80 aa = 0; bb = 1; ccin = 1;
15        #80 aa = 0; bb = 1; ccin = 0;
16        #100 $stop;
17    end
18 endmodule
```

Simulation Result

 

As you can see, the worst-case delay for s and co output are **46ns** and **31ns**.

N-bit Ripple Carry Adder (Structural)


N-bit Ripple Carry Adder has been implemented using generate statement.

```
1 `timescale 1ns/1ns
2 module RCA_structural #( parameter SIZE = 8 )
3     (input [SIZE-1:0] A,B,input cin, output [SIZE-1:0] sum,output co);
4     wire [0:SIZE] carry_in;
5     assign carry_in[0] = cin;
6     genvar i;
7     generate
8         for(i = 0; i < SIZE; i = i + 1) begin
9             FA_structural XX(A[i],B[i],carry_in[i],sum[i],carry_in[i+1]);
10        end
11    endgenerate
12    assign co = carry_in[SIZE];
13 endmodule
```

Testbench

```
1
2 `timescale 1ns/1ns
3 module RCA_structural_TB();
4     reg [7:0] aa,bb;
5     reg ccin;
6     wire cout;
7     wire [7:0] sum;
8     RCA_structural #(8) CUT1 (aa,bb,ccin,sum,cout);
9
10    initial begin
11        #10 aa = 8'b00000001; bb = 8'b00000000; ccin = 1;
12        #371 aa = 8'b00000001; bb = 8'b00000011; ccin = 0;
13        #371 aa = 8'b001111001; bb = 8'b10000111; ccin = 1;
14        #371 aa = 8'b11111111; bb = 8'b00000001; ccin = 0;
15        #371 aa = 8'b11111111; bb = 8'b00000001; ccin = 0;
16        #371 aa = 8'b11111111; bb = 8'b10000001; ccin = 1;
17        #203 $stop;
18    end
19 endmodule
```

Simulation Result

 

In a 8-bit RCA, 8 Full-Adder are cascaded together. We know the worst-case delay of FA is 46ns.

So at most, it should take $46 \times 8 = 368\text{ns}$ in the worst-case.

Problem 2

Verilog Code

In problem 1, we calculated worst-case delay of FA which is 46ns. So n-bit Ripple Carry Adder has $46 \times n$ delay at most.


```
1 `timescale 1ns/1ns
2 module RCA_behavioural #(parameter n = 8)
3     (input [n-1:0] A,B,input cin,output [n-1:0] s, output co);
4     assign #(46*n) {co,s} = A + B + cin;
5 endmodule
```

Problem 3

Testbench

```
1
2 `timescale 1ns/1ns
3 module RCA_behavioural_TB();
4     reg [3:0] aa,bb;
5     reg ccin;
6     wire cout;
7     wire [3:0] sum;
8     RCA_behavioural #(4) CUT1 (aa,bb,ccin,sum,cout);
9
10    initial begin
11        #10 aa = 4'b0001; bb = 4'b0000; ccin = 1;
12        #203 aa = 4'b1111; bb = 4'b0000; ccin = 1;
13        #203 aa = 4'b1110; bb = 4'b0001; ccin = 1;
14        #203 aa = 4'b1000; bb = 4'b0001; ccin = 0;
15        #203 aa = 4'b1111; bb = 4'b0001; ccin = 1;
16        #203 aa = 4'b1000; bb = 4'b1111; ccin = 0;
17        repeat(10) #203 aa = $random(); bb = $random(); ccin = $random();
18        #203 $stop;
19    end
20 endmodule
```

Simulation Result

 

Problem 4

Circuit Diagram

????????

Verilog Code

```
1  `timescale 1ns/1ns
2  module OnesCounter #(parameter levels = 6) (input [0 : 2 ** (levels + 1) - 2] in, output [levels : 0] out);
3      wire c[1:2**levels];
4      wire [levels-1:0] w[1:2**levels];
5      assign out = {c[1], w[1]};
6      genvar i, j;
7      generate
8          for(i = 0; i < levels; i = i + 1) begin
9              for(j = 2 ** i; j < 2 ** (i + 1); j = j + 1) begin
10                 if(i < levels - 1)
11                     RCA_behavioural #(levels - i) XX({c[2 * j], w[2 * j][levels - i - 2 : 0]}, {c[2 * j + 1],
12                     w[2 * j + 1][levels - i - 2 : 0]}, in[j - 1], w[j][levels - i - 1 : 0], c[j]);
13                 else
14                     RCA_behavioural #(levels - i) XX(in[2 * j - 1], in[2 * j + 1 - 1], in[j - 1],
15                     w[j][levels - i - 1 : 0], c[j]);
16             end
17         end
18     endgenerate
19 endmodule
```


Testbench

```

1 `timescale 1ns / 1ns
2 module OnesCounterTB();
3     reg [126 : 0] numb;
4     wire [6 : 0] out;
5     OnesCounter #6 onecounter(numb,out);
6     initial begin
7         //Marching-1
8         #1000 numb = 127'b0;
9         repeat(127*2) begin
10             #1000 numb = {~numb[0], numb[126 : 1]};
11         end
12
13         //Other tests
14         #1000 numb = 127'b1011111000111111111111111000000;
15         #1000 numb = 127'b101111100011111111111111100001100110011;
16         #1000 numb = 127'b10111111000111111111111110000001111111111;
17         #1000 numb = 127'b1011111000111111111111111000000111111111000000000000001111111111;
18         #1000 $stop;
19     end
20 endmodule

```

Simulation Result

 

Verilog Code

```

1 `timescale 1ns/1ns
2 module ones_counter_behavioural #(parameter n = 127)
3     (input [n-1:0] A,output reg [n-1:0] count);
4
5     integer i;
6     always @ (A) begin
7         count = 127'b0;
8         #1000
9         for (i = 0; i < n; i = i + 1) begin
10             if (A[i] == 1'b1)
11                 count = count + 1;
12         end
13     end
14 endmodule

```


Testbench

```

1 | timescale 1ns / 1ns
2 | module ones_counter_behavioural_TB();
3 |     reg [126 : 0] numb;
4 |     wire [6 : 0] out;
5 |     ones_counter_behavioural onecounter(numb,out);
6 |     initial begin
7 |         //Marching-1
8 |         #1200 numb = 127'b0;
9 |         repeat(127*2) begin
10 |             #1200 numb = {~numb[0], numb[126 : 1]};
11 |         end
12 |
13 |         //Other tests
14 |         #1200 numb = 127'b1011111000111111111111111000000;
15 |         #1200 numb = 127'b101111100011111111111111100001100110011;
16 |         #1200 numb = 127'b10111110001111111111111110000001111111111;
17 |         #1200 numb = 127'b101111100011111111111111100000011111111100000000000000111111111;
18 |         #1200 $stop;
19 |     end
20 | endmodule

```

Simulation Result

 

The output of problem 5 and 6 are the same.

Problem 7

The synthesized file can be found in `OnesCounter2_Synth.v`

Here you can see the number of wires and cells needed for this synthesis :

```
Removed 0 unused modules.

2.23. Printing statistics.

=== ones_counter_behavioural ===

Number of wires:          39436
Number of wire bits:      39688
Number of public wires:   2
Number of public wire bits: 254
Number of memories:       0
Number of memory bits:    0
Number of processes:      0
Number of cells:          39561
  $_AND_                   3451
  $_AOI3_                   2
  $_MUX_                    5445
  $_NAND_                   7901
  $_NOR_                    4245
  $_NOT_                    1942
  $_OAI3_                   5440
  $_OR_                     3136
  $_XNOR_                   7061
  $_XOR_                    938

2.24. Executing CHECK pass (checking for obvious problems).
checking module ones_counter_behavioural..
found and reported 0 problems.

yosys> _
```

Problem 4 and 7 comparison

In problem 4, we have one 6-bit RCA, two 5-bit RCA, four 4-bit RCA, eight 3-bit RCA, sixteen 2-bit RCA and thirty-two 1-bit Adder.

Full-Adder circuit contains 5 gates and a n-bit RCA contains n FA pieces. So n-bit RCA contains $5n$ logic gates.

Number of gates used in problem4 :

$$5*6 + 2*5*5 + 4*5*4 + 8*5*3 + 16*5*2 + 32*5*1 = 600$$

We only used 600 logic gates, whereas problem 7 used 40000 logic gates!