



UNIVERSITY OF TEHRAN

Report for Computer Assignment 4

Latches, flip-flops, and a little beyond


Instructor : Dr. Navabi

Danial Saeedi

 Problem 1

Circuit Diagram

The worst-case delay of NAND according to its delays is $4 + 4 = 8\text{ns}$.




Verilog Code

```
1 `timescale 1ns/1ns
2 module SR_Latch(input S, R, CLK, output Q, Q_bar);
3     wire g,p;
4     nand #8 G1(g,S,CLK);
5     nand #8 G2(p,R,CLK);
6
7     nand #8 G3(Q,g,Q_bar);
8     nand #8 G4(Q_bar,p,Q);
9 endmodule
```

Problem 2


Testbench

```
1  `timescale 1ns/1ns
2  module SR_Gated_TB();
3      reg SS, RR;
4      reg cclk=1'b0;
5      wire QQ, QQ_prime;
6
7      SR_Latch CUT1 (SS, RR, cclk, QQ, QQ_prime);
8
9      always #80 cclk=~cclk;
10
11     initial begin
12         #89 SS=1;RR=0;
13         #89 SS=0;RR=1;
14         #89 SS=1;
15         #89 SS=1;RR=0;
16         #89 SS=1;RR=1;
17         #89 SS=0;RR=1;
18         #89 SS=1;RR=1;
19         #89 SS=0;RR=0;
20         #89 $stop;
21     end
22 endmodule
```

 

Problem 3

Circuit Diagram

 


Verilog Code

```
1 `timescale 1ns/1ns
2 module D_Latch(input D, clk, output Q, Q_BAR);
3     wire D_BAR;
4
5     not #6 G1(D_BAR,D);
6
7     SR_Latch CUT1(D, D_BAR, clk, Q, Q_BAR);
8 endmodule
```

Testbench


```
1 `timescale 1ns/1ns
2 module D_Latch_TB();
3     reg DD;
4     reg cclk=1;
5     wire QQ,QQ_bar;
6
7     D_Latch CUT1 (DD, cclk, QQ, QQ_bar);
8
9     always #80 cclk=~cclk;
10
11     initial begin
12         #89 DD=1;
13         #89 DD=0;
14         #89 DD=0;
15         #89 DD=1;
16         #89 DD=1;
17         #89 DD=1;
18         #89 DD=0;
19         repeat(20) #89 DD = ~DD;
20         #89 $stop;
21     end
22 endmodule
```

Simulation Result

 

Problem 4

Circuit Diagram

 

Verilog Code


```
1 `timescale 1ns/1ns
2 module shift_register(input sin,clk, output [7:0] PO);
3     wire [8:0] Q;
4     wire [8:0] Q_BAR;
5     assign Q[8] = sin;
6     assign PO[0] = Q[0];
7     genvar i;
8     generate
9         for (i=0;i<8;i=i+1) begin: I0
10             D_Latch XX(Q[i+1],clk,Q[i],Q_BAR[i]);
11             assign PO[i]=Q[i];
12         end
13     endgenerate
14 endmoduleA
```

Problem 5

Testbench

```
1  `timescale 1ns/1ns
2  module shift_register_TB();
3      reg ssin;
4      reg cclk = 1'b1;
5      //Primary Output
6      wire [7:0] PPO;
7
8      shift_register CUT1(ssin, cclk, PPO);
9
10     always #600 ssin=$random;
11     always #500 cclk=~cclk;
12     initial begin
13         #12000 $stop;
14     end
15 endmodule
```


Simulation Result

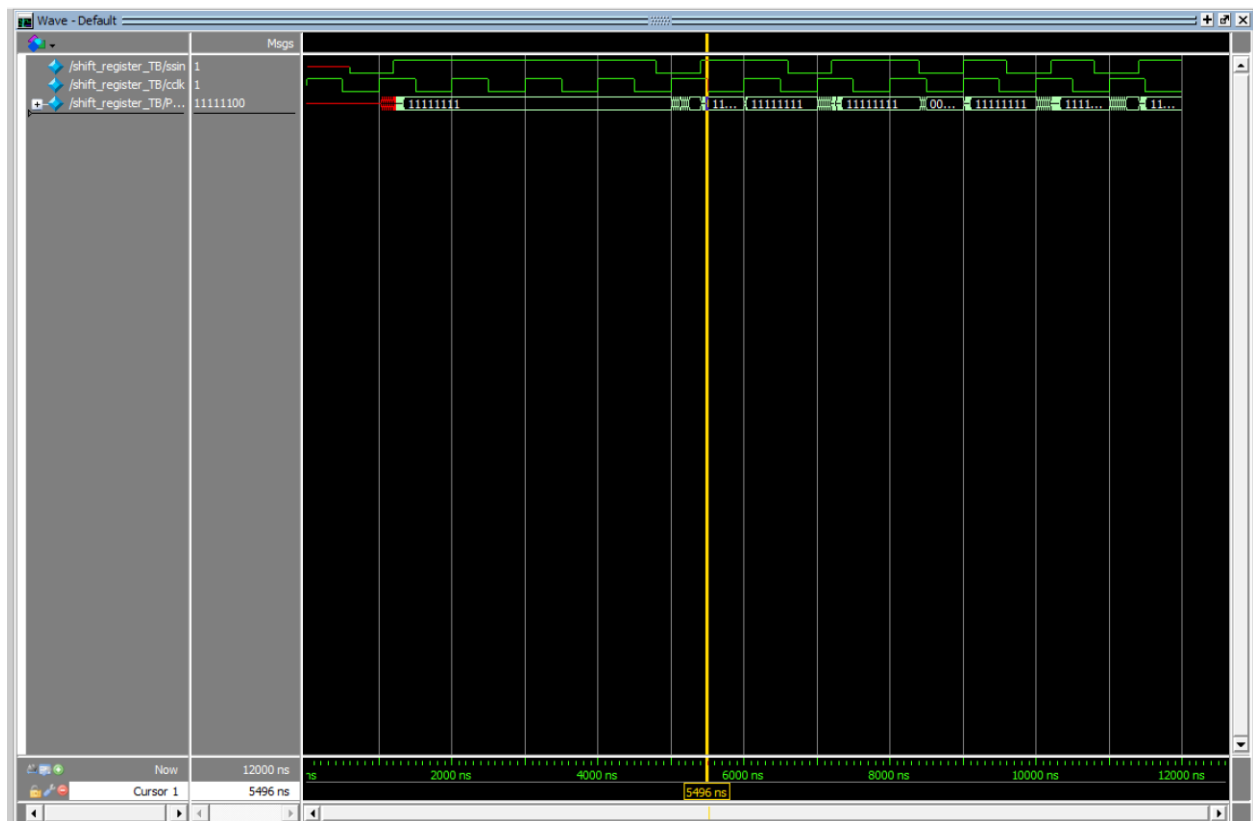

As you can see, this circuit **doesn't** work because it has **transparency** issue.

Problem 6

Circuit Diagram

 

Verilog Code

```
1 `timescale 1ns/1ns
2 module DFF_MS(input D, clk, output Q,Q_bar);
3     wire q1,q1_bar,clk_not;
4     D_Latch D1(D,clk,q1,q1_bar);
5
6     not #6 G1(clk_not,clk);
7     D_Latch D2(q1,clk_not,Q,Q_bar);
8 endmodule
```


Testbench

```
1  `timescale 1ns/1ns
2  module DFF_MS_TB();
3      reg DD;
4      reg cclk=1'b1;
5      wire QQ,QQ_bar;
6
7      DFF_MS CUT(DD, cclk, QQ, QQ_bar);
8
9      always #100 cclk=~cclk;
10
11     initial begin
12         #150 DD=1;
13         #150 DD=0;
14         #150 DD=0;
15         #150 DD=1;
16         #150 $stop;
17     end
18 endmodule
```

Simulation Result



Problem 7


Verilog Code

```
1 `timescale 1ns/1ns
2 module DFF_MS_RST(input D, clk, rst, output Q,Q_bar);
3     wire D2;
4     assign D2 = D & ~rst;
5
6     DFF_MS CUT(D2, clk, Q);
7 endmodule
```

Testbench


```
1 `timescale 1ns/1ns
2 module DFF_MS_RST_TB();
3     reg DD;
4     reg cclk=1'b1;
5     reg reset = 1'b0;
6     wire QQ,QQ_bar;
7
8     DFF_MS_RST CUT(DD, cclk, reset, QQ, QQ_bar);
9
10    always #100 cclk=~cclk;
11
12    initial begin
13        #150 DD=1;
14        #150 DD=0;
15        #150 DD=1; reset = 1;
16        #150 DD=1;
17        #150 DD=1; reset = 0;
18        #150 $stop;
19    end
20 endmodule
```

Simulation Result

 

Problem 8

Circuit Diagram

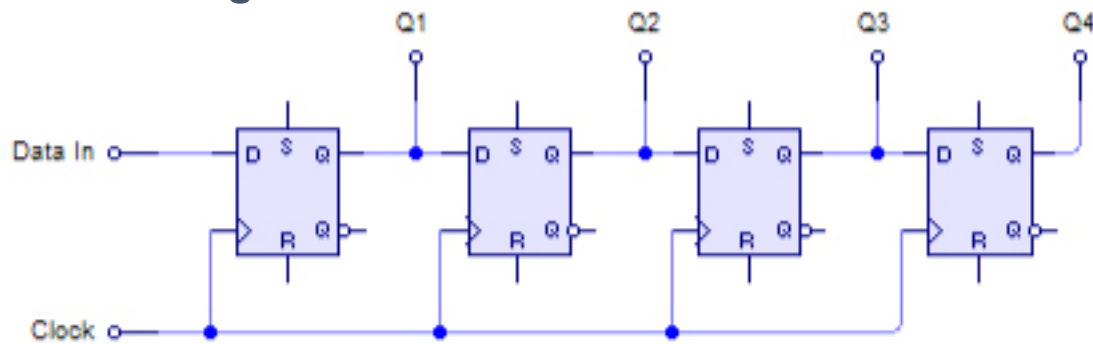


Verilog Code

```
1 `timescale 1ns/1ns
2 module shift_register2(input sin,clk,rst, output [7:0] P0);
3     wire [8:0] Q;
4     wire [8:0] Q_BAR;
5     assign Q[8] = sin;
6     assign P0[0] = Q[0];
7     genvar i;
8     generate
9         for (i=0;i<8;i=i+1) begin: I0
10             DFF_MS_RST XX(Q[i+1],clk, rst ,Q[i],Q_BAR[i]);
11             assign P0[i]=Q[i];
12         end
13     endgenerate
14 endmodule
```

Testbench

```
1 `timescale 1ns/1ns
2 module shift_register2_TB();
3     reg ssin;
4     reg cclk = 1'b1;
5     reg reset = 1'b0;
6     //Primary Output
7     wire [7:0] PPO;
8
9     shift_register2 CUT1(ssin, cclk, reset , PPO);
10
11     always #600 ssin=$random;
12     always #500 cclk=~cclk;
13     initial begin
14         #12000 $stop;
15     end
16 endmodule
```

Simulation Result

 

As you can see, this circuit works because it doesn't have transparency issue unlike problem 4.

Problem 9


Verilog Code

```
1 `timescale 1ns/1ns
2 module shift_register2(input sin, input clk,rs output reg [7:0] P0);
3     always @(posedge clk, posedge rs) begin
4         if (rs)
5             PO <= 8'b0;
6         else
7             PO <= {sin, PO[7:1]};
8     end
9 endmodule
```

Testbench


```
1 `timescale 1ns/1ns
2 module shift_register3_TB();
3     reg ssin;
4     reg cclk = 1'b1;
5     reg reset = 1'b0;
6     //Primary Output
7     wire [7:0] PPO;
8
9     shift_register3 CUT1(ssin, cclk, reset , PPO);
10
11     always #600 ssin=$random;
12     always #500 cclk=~cclk;
13     initial begin
14         #12000 $stop;
15     end
16 endmodule
```

Simulation Result

 

Problem 10

Circuit Diagram

 

Verilog Code

```
1 // LFSR with  $x^8+x^7+x^6+x^3+1$  polynomial
2 module LFSR#(parameter N = 8)( input clk, reset, output [N:0] q);
3
4     reg [N:0] r_reg;
5     wire [N:0] r_next;
6     wire feedback_value;
7
8     always @(posedge clk, posedge reset)
9     begin
10         if (reset)
11         begin
12             r_reg <= 1;
13         end
14         else if (clk == 1'b1)
15         begin
16             r_reg <= r_next;
17         end
18     end
19     assign feedback_value = r_reg[N] ^ r_reg[N-1] ^ r_reg[N-2] ^ r_reg[N-3] ^ r_reg[N-4];
20     assign r_next = {feedback_value, r_reg[N:1]};
21     assign q = r_reg;
22 endmodule
```

Testbench

```
1 `timescale 1ns/1ns
2 module LFSR_TB();
3     reg cclk = 1'b0;
4     reg rrs = 1'b0;
5     wire [8:0] q;
6     LFSR CUT2(cclk,rrs,q);
7     always #100 cclk = ~cclk;
8     initial begin
9         #50 rrs = 1;
10        #50 rrs = 0;
11        #2000 $stop;
12    end
13 endmodule
```

Simulation Result

